
UM-SJTU JOINT INSTITUTE
PHYSICS LABORATORY
(VP241)

LABORATORY REPORT

EXERCISE 5
RC, RL AND RLC CIRCUIT

Name: Haoming Zhu ID: 520021910145 Group: 1

Date: 2021.12.3

Contents

1	Introduction	1
1.1	Objective	1
1.2	RC Series Circuit	1
1.2.1	<i>RL</i> Series Circuit	1
1.2.2	RLC Series Circuit	1
1.3	<i>RLC</i> Resonant Circuit	2
1.3.1	Phase Shift and Resonance Frequency	2
1.3.2	Resonance	3
1.3.3	Quality Factor in Resonant Circuits	3
2	Apparatus	3
3	Measurement Procedure	4
3.1	<i>RC</i> , <i>RL</i> Series Circuit	4
3.2	<i>RLC</i> Series Circuit	4
3.3	<i>RLC</i> Resonant Circuit	4
4	Results	4
4.1	<i>RC</i> Series Circuit	4
4.2	<i>RL</i> Series Circuit	5
4.3	<i>RLC</i> Series Circuit	6
4.4	<i>RLC</i> Resonant Circuit	8
4.4.1	Relation of I/I_m vs. f/f_0 and φ vs. f/f_0	8
4.4.2	Quality Factor Q	10
5	Conclusions and Discussion	11
5.1	<i>RC</i> , <i>RL</i> and <i>RLC</i> Series Circuits	11
5.2	<i>RLC</i> Resonant Circuit	11
5.3	Suggestions and Improvement	12
5.4	Conclusions	12
A	Uncertainty Analysis	13
A.1	<i>RC</i> Circuit	13
A.2	<i>RL</i> Circuit	13
A.3	Uncertainty of Data for <i>RLC</i> Circuit	14
A.4	<i>RLC</i> Resonant Circuit	14
A.4.1	f/f_0	14
A.4.2	I/I_m	14
A.4.3	φ_{theo}	15
A.4.4	φ_{ex}	15
A.4.5	f_0_{theo}	16
A.4.6	Q_{exp}	16
A.4.7	Q_{theo}	17
B	Data Sheet	17

1 Introduction

1.1 Objective

The objective of this lab is to study the properties of RC, RL, and RLC circuits. The charging and discharging process of each circuit is particularly studied. Also, the resonance phenomenon of RLC circuit is explored by studying the resonance frequency and quality factor.

1.2 RC Series Circuit

An *RC* circuit consists of a capacitor, a resistor and a current source. For the charging process applying Kirchhoff's loop rule, we get

$$RC \frac{dU_C}{dt} + U_C = \mathcal{E} \quad (1)$$

solve the equation, the voltage across the capacitor is then

$$U_C = \mathcal{E}(1 - e^{-\frac{t}{RC}}) \quad \text{and} \quad U_R = iR = \mathcal{E}e^{-\frac{t}{RC}}$$

For the discharging process, we just need to replace the *rhs* of Eq. (1) with 0, then we can get

$$U_C = U_R = \mathcal{E}e^{-\frac{t}{RC}}$$

The *time constant* of the circuit is defined to be $\tau = RC$. The half-life period is defined to be the time needed for U_C to decrease to half of the initial value or increase to half of the terminal value. By their definition and the expression of U_C , it can be derived that

$$T_{1/2} = \tau \ln 2. \quad (2)$$

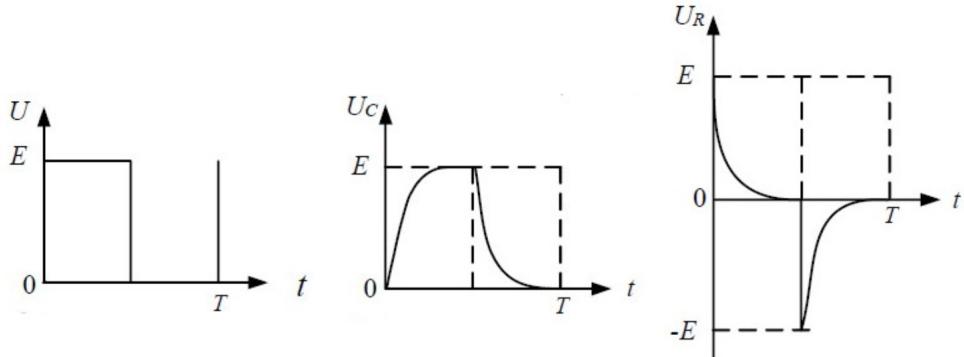


Figure 1: Charging/discharging curves for a *RC* series circuit.

1.2.1 *RL* Series Circuit

An *RL* consists of an inductor and a resistance. Similarly, the time constant $\tau = \frac{L}{R}$ and still

$$T_{1/2} = \tau \ln 2. \quad (3)$$

1.2.2 *RLC* Series Circuit

An *RLC* circuit consists of an inductor, a capacitor and a resistor. By KVL, we can obtain a second order ordinary differential equation *w.r.t.* the voltage in the loop:

$$LC \frac{d^2U_C}{dt^2} + RC \frac{dU_C}{dt} + U_C = \mathcal{E}, \quad (4)$$

Dividing both sides of the equation by LC and introducing the symbols

$$\beta = \frac{R}{2L}, \quad \text{and} \quad \omega_0 = \frac{1}{\sqrt{LC}},$$

it can be rewritten as

$$\frac{d^2U_C}{dt^2} + 2\beta \frac{dU_C}{dt} + \omega_0^2 U_C = \omega_0^2 \mathcal{E}, \quad (5)$$

with initial conditions

$$U_C(t=0) = 0 \quad \text{and} \quad \left. \frac{dU_C}{dt} \right|_{t=0} = 0.$$

Given different values of β and ω_0 , there are three regimes, as implied by the solution of the complementary homogeneous equation:

► If $\beta^2 - \omega_0^2 < 0$ (weak damping), the system is in the underdamped regime and the solution to the initial value problem is of the form

$$U_C = \mathcal{E} - \mathcal{E}e^{-\beta t}(\cos \omega t + \frac{\beta}{\omega} \sin \omega t),$$

where $\omega = \sqrt{\omega_0^2 - \beta^2}$.

► If $\beta^2 - \omega_0^2 > 0$ (strong damping), the system is in the overdamped regime with the solution of the form

$$U_C = \mathcal{E} - \frac{\mathcal{E}}{2\gamma} e^{-\beta t}[(\beta + \gamma)e^{\gamma t} - (\beta - \gamma)e^{-\gamma t}],$$

where $\gamma = \sqrt{\beta^2 - \omega_0^2}$.

► Finally, if $\beta^2 - \omega_0^2 = 0$, the system is said to be critically damped, and

$$U_C = \mathcal{E} - \mathcal{E}(1 + \beta t)e^{-\beta t}.$$

When the RLC circuit system is **critically damped**, the time constant and can be obtained using $T_{0.264}$ through

$$\tau = \frac{T_{0.264}}{1.00} = \sqrt{LC}. \quad (6)$$

The three regimes are shown below.

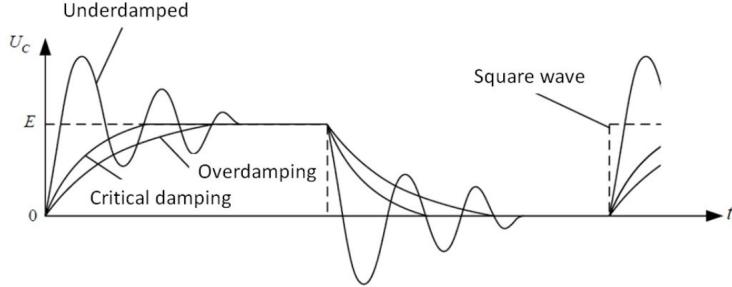


Figure 2: Three different regimes of transient processes in a RLC series circuit.

1.3 RLC Resonant Circuit

1.3.1 Phase Shift and Resonance Frequency

We know that in AC circuit

$$Z_R = R \quad Z_C = \frac{j}{\omega C} \quad Z_L = j\omega L$$

Then according to the rule of complex magnitude, the total impedance is

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2},$$

with the phase difference between the current and the voltage in the circuit

$$\varphi = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right). \quad (7)$$

1.3.2 Resonance

If the frequency of the input signal provided by the source satisfies

$$\omega_0 L = \frac{1}{\omega_0 C}, \quad \text{which gives} \quad \omega_0 = \frac{1}{\sqrt{LC}},$$

the total impedance will reach a minimum, $Z_0 = R$. Correspondingly, the current reaches its maximum, $I_m = U/R$. Then the circuit is said to be at resonance. The theoretical resonance frequency is then

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}, \quad (8)$$

1.3.3 Quality Factor in Resonant Circuits

For a circuit driven at the resonance frequency, the ratio of U_L (or U_C) to U is called the quality factor Q of a resonant circuits

$$Q = \frac{U_L}{U} = \frac{\omega_0 L}{R} \quad \text{or} \quad Q = \frac{U_C}{U} = \frac{1}{\omega_0 R C} = \frac{\sqrt{LC}}{RC}. \quad (9)$$

The quality factor is then

$$Q = \frac{f_0}{f_2 - f_1}, \quad (10)$$

where f_1 and f_2 are two frequencies such that $I(f_1) = I(f_2) = I_m/\sqrt{2}$.

2 Apparatus

The measurement devices consists of a signal generator, an oscilloscope, a digital multimeter, a wiring board, a fixed resistor 100Ω (2 W), a variable resistor $2 \text{ k}\Omega$ (2 W), two capacitors $0.47 \mu\text{F}$ and $0.1 \mu\text{F}$, and two inductors (10 mH and 33 mH).

The precisions of the apparatus are shown below. The 10 mH inductor used in this lab is precise, and we consider it as 0 uncertainty.

Apparatus	Quantity measured	Uncertainty
Signal generator	Frequency	0.001 Hz
	Amplitude	0.001 V _{pp}
Oscilloscope	Time	0.01/0.001 μs
	Voltage	0.02/0.002 V _{pp}
Digital multimeter	Resistance	0.01 Ω
	Capacitance	0.01 nF

Table 1: Precision of the measurement instruments.

3 Measurement Procedure

3.1 RC , RL Series Circuit

In this part, the wave forms of RC and RL circuits are studied.

First, I chose a capacitor labelled with $0.1 \mu F$ and a inductor labelled with $10 mF$ to connect with a resistor labelled with 100Ω to form two circuits respectively. Note that in the RC circuit, the voltage across the capacitor is measured through oscilloscope, while in the RL circuit the voltage across the resistor is measured.

Next, I adjusted the oscilloscope and measured $T_{0.264}$ for the two circuits respectively. Then, the time constant can be calculated and compared with the theoretical value. Also, I took screen shots for the two wave forms.

3.2 RLC Series Circuit

In this part, the wave forms of RLC circuit under different regimes are studied, including under-damped, critically damped, and over-damped regimes.

First, I connected the $0.1\mu F$ capacitor, the $10 mF$ inductor and a rheostat in series. Then, I adjusted the rheostat to obtain the three regimes and took three screen shots.

Next, I adjusted the rheostat to obtain critical damped again and find the corresponding parameters of $T_{0.264}$ to find the time constant.

3.3 RLC Resonant Circuit

In this part, the RLC circuit under resonance is studied to find the quality factor Q .

First, the power source's wave form is shifted to sinusoidal waves. Then, I adjusted the input frequency until the circuit reach the resonant state and recorded the frequency. Next, below and beyond the resonant frequency, I took another 20 frequencies that have same voltages in symmetry. Finally, I lotted the graphs f/f_0 vs. I/I_m and f/f_0 vs. φ to estimate the resonance frequency and calculate the quality factor Q .

4 Results

4.1 RC Series Circuit

The measured data for the RC series are shown in Table 2.

Quantity	Value
$R [\Omega]$	99.75 ± 0.01
$f [\text{Hz}]$	1000.000 ± 0.001
$C [\text{nF}]$	99.84 ± 0.01
$\mathcal{E} [\text{V}_{\text{pp}}]$	4.000 ± 0.001
$T_{1/2} [\mu\text{s}]$	7.000 ± 0.001

Table 2: $T_{1/2}$ measurement data for a RC series circuit.

According to Eq.(2), the experimental time constant τ can be calculated as

$$\tau = \frac{T_{1/2}}{\ln 2} = \frac{7.000}{\ln 2} = 10.0989 \pm 0.0014 [\mu\text{s}].$$

According to the capacitor and resistor used in the circuit, the theoretical value τ_{theo} for this RC circuit is

$$\tau_{\text{theo}} = RC = 99.75 \times 99.84 \times 10^{-3} = 9.96 \pm 0.10 [\mu\text{s}].$$

The relative deviation u_r is then

$$u_r = \frac{|\tau - \tau_{\text{theo}}|}{\tau_{\text{theo}}} \times 100\% = \frac{10.0989 - 9.96}{9.9590} \times 100\% = 1.4\%.$$

Figure 3 shows the wave form of the RC circuit.

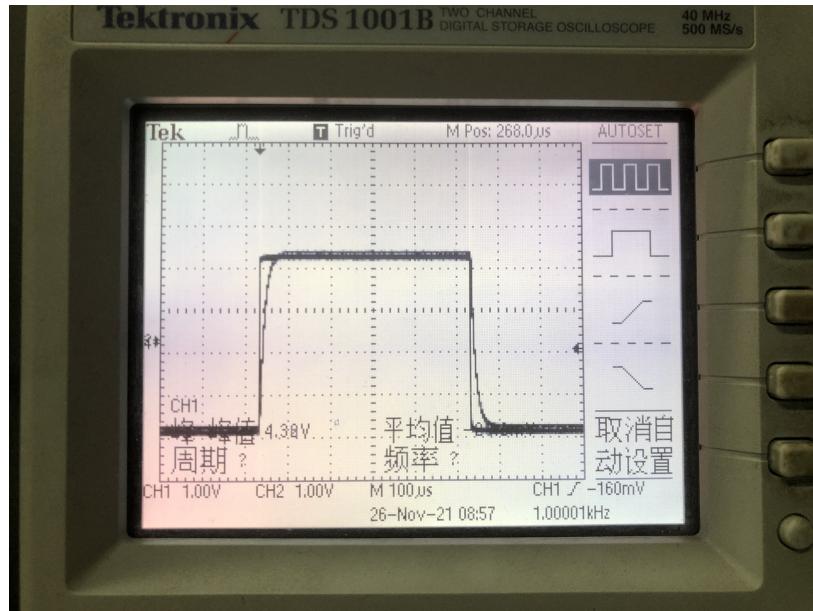


Figure 3: Wave form of a RC series circuit.

4.2 RL Series Circuit

The measured data for the RL series are shown in Table 3.

Quantity	Value
R [Ω]	99.75 ± 0.01
f [Hz]	1000.000 ± 0.001
L [H]	0.01 ± 0
\mathcal{E} [V _{pp}]	4.000 ± 0.001
$T_{1/2}$ [μs]	66.00 ± 0.01

Table 3: $T_{1/2}$ measurement data for a RL series circuit.

According to the Eq.(3), the experimental time constant τ can be calculated as

$$\tau = \frac{T_{1/2}}{\ln 2} = \frac{66.00}{\ln 2} = 95.218 \pm 0.014 \ [\mu\text{s}].$$

According to the inductor and resistor used in the circuit, the theoretical value τ_{theo} for this RL circuit is

$$\tau_{\text{theo}} = \frac{L}{R} = \frac{0.01}{99.75} \times 10^6 = 100.261 \pm 0.010 \ [\mu\text{s}].$$

The relative deviation u_r is then

$$u_r = \frac{|\tau - \tau_{\text{theo}}|}{\tau_{\text{theo}}} \times 100\% = \frac{100.261 - 95.218}{100.261} \times 100\% = 5\%.$$

Figure 4 shows the wave form of the RC circuit.



Figure 4: Wave form of a RL series circuit.

4.3 RLC Series Circuit

The measured data for the RLC circuit are shown in Table 4.

Quantity	Value
f [Hz]	1000.000 ± 0.001
C [nF]	99.84 ± 0.01
L [H]	0.01 ± 0
\mathcal{E} [V _{pp}]	4.000 ± 0.001
$T_{0.264}$ [μs]	30.00 ± 0.01

Table 4: $T_{1/2}$ measurement data for a critically damped RLC series circuit.

According to Eq.(6), the experimental time constant τ can be calculated as

$$\tau = T_{0.264} = 30.00 \pm 0.01 \text{ } [\mu\text{s}],$$


According to the elements used in the circuit, the theoretical value τ_{theo} for this RLC circuit is

$$\tau_{\text{theo}} = \sqrt{LC} = \sqrt{0.01 \times 99.82 \times 10^{-9}} \times 10^6 = 31.5975 \pm 0.0016 \text{ } [\mu\text{s}].$$


The relative deviation u_r is then

$$u_r = \frac{|\tau - \tau_{\text{theo}}|}{\tau_{\text{theo}}} \times 100\% = \frac{31.5943 - 30.00}{31.5943} \times 100\% = 5\%.$$


Figure 5 shows the three wave forms of different regimes of the RC circuit.

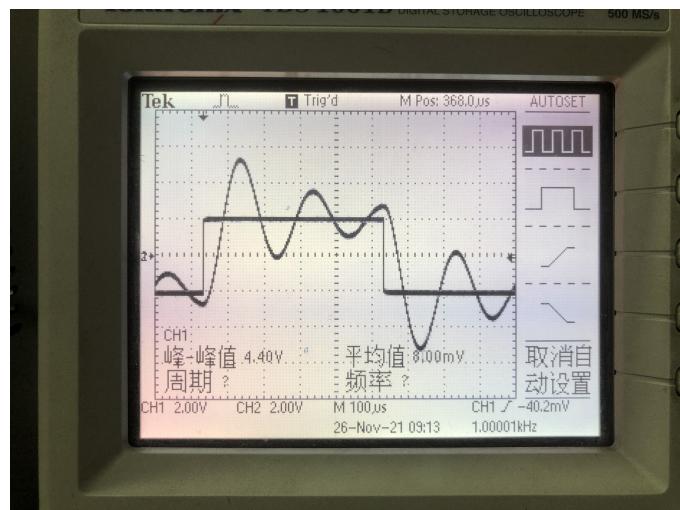

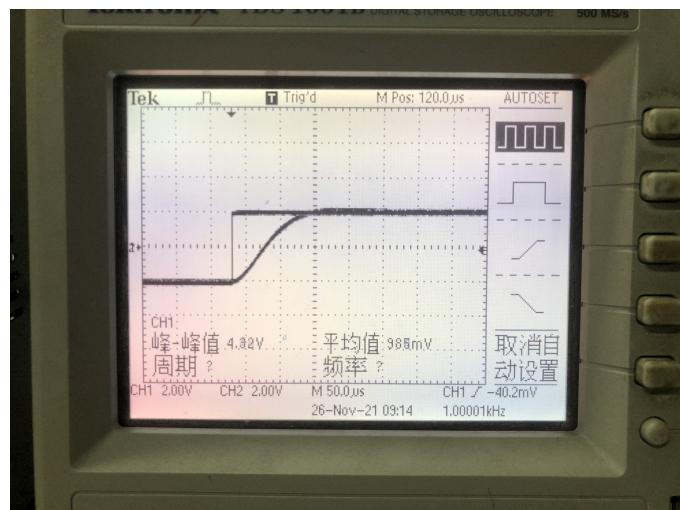(a) Under-damped regime of the RLC circuit.



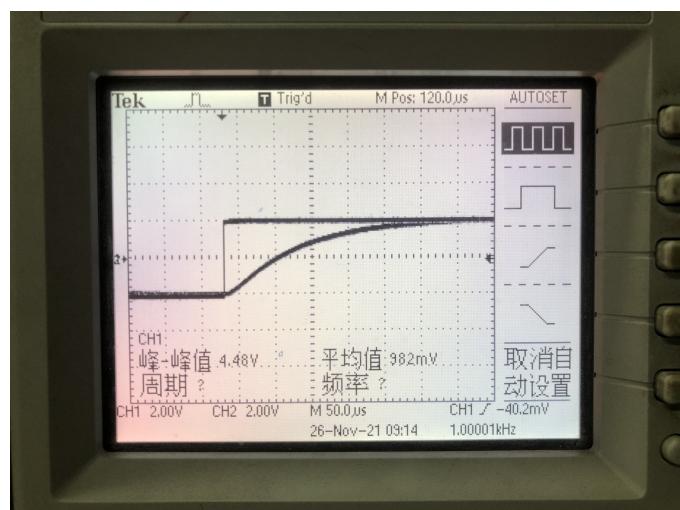(b) Critical-damped regime of the RLC circuit.



(c) Over-damped regime of the RLC circuit.

Figure 5: Wave forms of the RLC series circuit.

4.4 RLC Resonant Circuit

4.4.1 Relation of I/I_m vs. f/f_0 and φ vs. f/f_0

The measured data for the RLC resonant circuit are shown in Table 5.

Quantity	Value	
$R [\Omega]$	99.75 ± 0.01	
$C [nF]$	99.84 ± 0.01	
$L [H]$	0.01 ± 0	
$\mathcal{E} [V_{pp}]$	4.000 ± 0.001	
$f_0 [Hz]$	5029.000 ± 0.001	
	$U_R [V_{pp}] \pm 0.02 [V_{pp}]$	$f [Hz] \pm 0.001 [Hz]$
1	0.39	21420.000
2	0.78	11120.000
3	1.17	8600.000
4	1.56	7420.000
5	1.95	6730.000
6	2.34	6300.000
7	2.73	6000.000
8	3.12	5700.000
9	3.51	5450.000
10	3.66	5340.000
11	3.90	5029.000
12	3.66	4710.000
13	3.51	4640.000
14	3.12	4430.000
15	2.73	4230.000
16	2.34	4010.000
17	1.95	3740.000
18	1.56	3400.000
19	1.17	2920.000
20	0.78	2180.000
21	0.39	1900.000

Table 5: Measurement data for the U_R vs. f dependence for a RLC resonant circuit.

To study the properties of resonance, I/I_m vs. f/f_0 and φ vs. f/f_0 plots are needed.

To get the values of I/I_m , f/f_0 , and φ , take the first set of data as an example,

$$f/f_0 = \frac{21420.000}{5029.000} = 4.259 \pm 0.0000002,$$

$$I/I_m = U_R/U_m = \frac{0.39}{3.90} = 0.100 \pm 0.0014,$$

Note that ϕ has two calculation paths, denote them as theoretical value φ_{theo} and experimental value φ_{exp} , respectively, then,

$$\begin{aligned} \varphi_{theo} &= \tan^{-1} \left(\frac{2\pi f L - \frac{1}{2\pi f C}}{R} \right) \\ &= \tan^{-1} \left(\frac{2\pi \times 21420.000 \times 0.01 - \frac{1}{2\pi \times 21420.000 \times 99.84 \times 10^{-9}}}{99.75} \right) \\ &= 1.4925 \pm 0.00003 [\text{rad}], \end{aligned}$$

$$\varphi_{exp} = \cos^{-1} \frac{U_R}{U_m} = \cos^{-1} \frac{0.920}{3.90} = 1.3263 \pm 0.0014 [\text{rad}],$$

The rest of the results are shown in Table 6 below.

	I/I_m	u_{I/I_m}	f/f_0	u_{f/f_0}	φ_{theo} [rad]	$u_{\varphi_{\text{theo}}}$ [rad]	φ_{exp} [rad]	$u_{\varphi_{\text{exp}}}$ [rad]
1	0.100	0.005	4.2592961	0.0000009	1.4925	0.0008	1.471	0.005
2	0.200	0.005	2.2111752	0.0000005	1.393	0.002	1.369	0.005
3	0.300	0.005	1.7100815	0.0000004	1.297	0.003	1.266	0.006
4	0.400	0.006	1.4754424	0.0000004	1.193	0.003	1.159	0.006
5	0.500	0.006	1.3382382	0.0000003	1.079	0.004	1.047	0.007
6	0.600	0.006	1.2527341	0.0000003	0.961	0.005	0.927	0.007
7	0.700	0.006	1.1930801	0.0000003	0.840	0.005	0.795	0.009
8	0.800	0.007	1.1334261	0.0000003	0.667	0.005	0.644	0.011
9	0.900	0.007	1.0837145	0.0000003	0.464	0.004	0.451	0.016
10	0.938	0.007	1.0618413	0.0000003	0.355	0.003	0.353	0.020
11	1.000	0.007	1.0000000	0.0000003	-0.0100	0.0003	0	/
12	0.938	0.007	0.9365679	0.0000003	-0.403	0.004	-0.353	0.020
13	0.900	0.007	0.9226486	0.0000003	-0.481	0.004	-0.451	0.016
14	0.800	0.007	0.8808908	0.0000003	-0.685	0.005	-0.644	0.011
15	0.700	0.006	0.8411215	0.0000003	-0.839	0.005	-0.795	0.009
16	0.600	0.006	0.7973752	0.0000003	-0.970	0.005	-0.927	0.007
17	0.500	0.006	0.7436866	0.0000002	-1.090	0.004	-1.047	0.007
18	0.400	0.006	0.6760787	0.0000002	-1.198	0.003	-1.159	0.006
19	0.300	0.005	0.5806323	0.0000002	-1.302	0.003	-1.266	0.006
20	0.200	0.005	0.4334858	0.0000002	-1.404	0.002	-1.369	0.005
21	0.100	0.005	0.3778087	0.0000002	-1.4331	0.0014	-1.471	0.005

Table 6: Results for φ , f/f_0 and I/I_m .

Using **Origin**, the I/I_m vs. f/f_0 and $\varphi_{\text{theo}}, \varphi_{\text{ex}}$ vs. f/f_0 curves are plotted in Figure 6 and Figure 7.

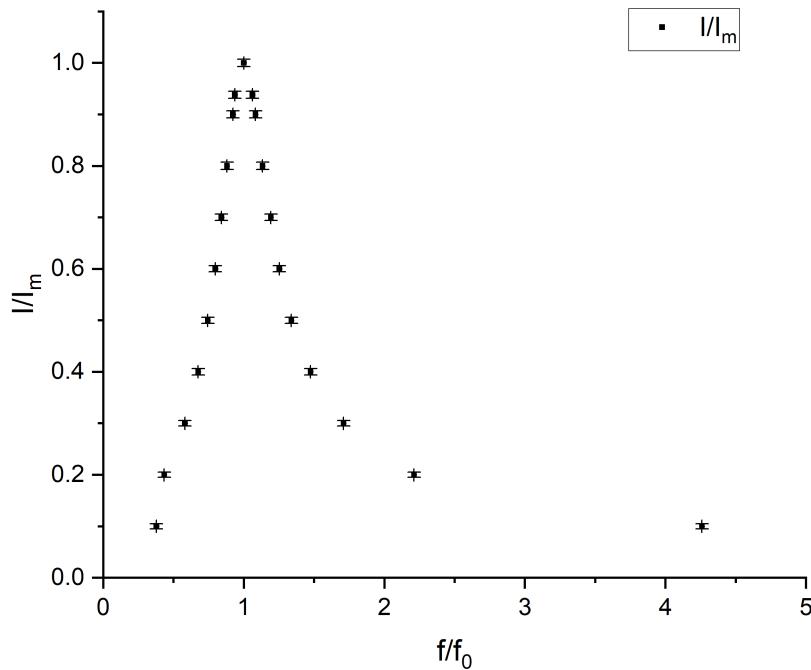


Figure 6: I/I_m vs. f/f_0 relation.

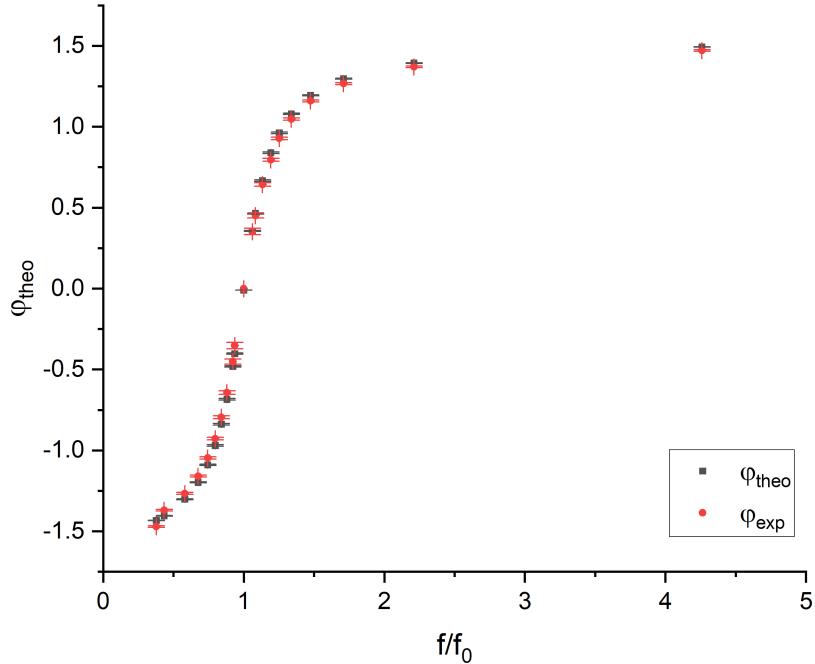


Figure 7: φ vs. f/f_0 relation.

4.4.2 Quality Factor Q

The experimentally resonance frequency is $f_0 = 5029.000 \pm 0.001$ [Hz]. According to Eq.(8), the theoretical resonance frequency is

$$f_{0\text{theo}} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.01 \times 99.84 \times 10^{-9}}} = 5037.0 \pm 0.3 \text{ [Hz]}$$

The relative deviation is then

$$u_r = \frac{|f_0 - f_{0\text{theo}}|}{f_{0\text{theo}}} \times 100\% = \frac{5037.0 - 5029.000}{5037.0} \times 100\% = 0.16\%.$$

According to Eq. (10), to find the quality factor Q , we first need to find out two frequencies f_1, f_2 such that $I/I_m \approx 1/\sqrt{2}$. Searching Table 5 and 6, we obtain that $f_1 = 4230$ Hz and $f_2 = 6000$ Hz. Then, the theoretical quality factor Q_{exp} can be found as

$$Q_{\text{exp}} = \frac{f_0}{f_2 - f_1} = \frac{5029.000}{6000.000 - 4230.000} = 2.841243 \pm 0.000002.$$

On the other hand, according to Eq.(9), the theoretical quality factor Q_{theo} can be found as

$$Q_{\text{theo}} = \frac{\sqrt{LC}}{RC} = \frac{\sqrt{0.01 \times 99.82 \times 10^{-9}}}{100.63 \times 99.82 \times 10^{-9}} = 3.1727 \pm 0.0003.$$

The relative error is thus

$$u_r = \frac{|Q_{\text{ex}} - Q_{\text{theo}}|}{Q_{\text{theo}}} \times 100\% = \frac{2.841243 - 3.1727}{3.1727} \times 100\% = 10\%.$$

5 Conclusions and Discussion

5.1 RC , RL and RLC Series Circuits

In this part, the properties of the wave forms of RC , RL and RLC series circuits are studied.

As is shown in Figure 3, when the input voltage changes abruptly at the edge of the square waves, the voltage across the capacitor will not suddenly change. Instead, it will experience exponential saturation until it reaches the input voltage. In steady state, the voltage across the capacitor eventually equals to the source voltage because the capacitor is considered to be open circuit in a DC circuit.

As is shown in Figure 4, when the input voltage changes abruptly at the edge of the square waves, the voltage across the resistor in the RL circuit will not suddenly change. As the current is directly proportional to the voltage across the resistor, we may conclude that the current in this circuit experiences exponential saturation. In steady state, the voltage across the resistor eventually equals to the source voltage because the inductor is considered to be no resistance in a DC circuit.

As is shown in Figure 5, when the circuit is underdamped, the voltage across the capacitor will oscillate before going to stability with decreasing amplitude (Figure 5(a)). When the circuit is critically damped, the voltage goes to stability rapidly (Figure 5(b)), and if increasing the rheostat, it will turn into underdamped regime. When the circuit is overdamped, the voltage goes to stability just like to wave form of the critically damped circuit. However, the critically damped circuit will go to steady state faster compared with the overdamped circuit (Figure 5(c)).

Then about the time constant, the theoretical time constants and experimental tie constants of the three regime are compiled together in Table 7 below:

	Experimental τ [μs]	Theoretical τ_{theo} [μs]	Relative error
RC circuit	10.0989 ± 0.0014	9.9590 ± 0.0014	1.4%
RL circuit	95.218 ± 0.014	103.874 ± 0.010	5%
RLC circuit	30.00 ± 0.01	31.5943 ± 0.0016	5%

Table 7: Result of time constant in RC , RL and RLC series circuits.

In general, three circuits' experimental results are close to the theoretical ones with acceptable errors.

Still, the minor errors may comes from the inaccuracy of the oscilloscope. When I was trying to shift the cursor so that the voltage difference reaches a certain value, due to the instability of the voltage, it is hard to precisely hit the expected point exactly, causing errors.

5.2 RLC Resonant Circuit

In the second part of the experiment, the RLC resonance circuit are studied.

Figure 6 shows the amplitude-frequency relation. From the figure, we can see that the amplitude maximized at resonance frequency, and decreases on the other sides. Then we can infer that when $f \rightarrow 0$, the current would approach 0; and as $f \rightarrow \infty$, the current would also approach 0.

Figure 7 compares the theoretical and experimental phase differences in frequency domain. Both of them match the shape of the function of *arctangent*. And the two curves are quite close. In general, the phase difference matches with theory quite well.

The experimental and theoretical results of resonance frequency f_0 and quality factor Q are summarized in Table Table 8.

	Experimental	Theoretical	Relative error
f_0 [Hz]	5029.000 ± 0.001	5037.0 ± 0.2	0.16%
Q	2.841243 ± 0.000003	3.1727 ± 0.0004	10%

Table 8: Result of resonance frequency and quality factor.

The experimental result of the resonance frequency is quite close to the theoretical one, which can be considered to be successful.

However, the experimental result of the quality factor is not that satisfying, with relative errors up to 10%. The possible reasons for such big error are listed below:

1. Theoretically, we need to choose two frequencies f_1, f_2 such that $I/I_m = 1/\sqrt{2}$. However, there is no set of data measured exactly at the point $I/I_m = 1/\sqrt{2}$ and we can only choose the data most close to that point, whose deviation causing errors.
2. When the frequency gets farther from the resonance frequency, the voltage becomes less sensitive to the changing frequency. Therefore the two frequencies chosen might not be that accurate, causing errors.

5.3 Suggestions and Improvement

The following suggestions may help to improve the experiment:

1. If possible, replace the oscilloscope with one with high resolution like what we use in VE215's lab.
2. Otherwise, the measured value of U_R is not stable, one possible solution is to measure the values for more times, for instance, 3 times, and take the averages as results.
3. To find the quality factor Q more precisely, I suggest to calculate the theoretical value first and then set the frequencies based on the theoretical voltage (current). In this way we can directly get the data point we need to use in the calculation of quality factor.

5.4 Conclusions

In this lab, the waveforms of the RC , RL and RLC series circuits are studied and the corresponding time constants are found out. Then, the resonance phenomenon is studied. The corresponding curves are plotted using Origin and the resonance frequency and the quality factor is estimated. Most of the results got in the experiment are close to the theoretical ones. In general, the objectives of lab are fulfilled.

References

- [1] VP241 Exercise 5: RC, RL, and RLC Circuits, UM-SJTU Joint Institute.

A Uncertainty Analysis

A.1 RC Circuit

The experimental value of the time constant is given by

$$\tau = \frac{T_{1/2}}{\ln 2}.$$

So, the uncertainty is

$$u_\tau = \left| \frac{d}{d(T_{1/2})} \left(\frac{T_{1/2}}{\ln 2} \right) u_{T_{1/2}} \right| = \frac{u_{T_{1/2}}}{\ln 2}.$$

Here the uncertainty of $T_{1/2}$ is $0.001[\mu s]$, so the uncertainty of τ is

$$u_\tau = \frac{0.001}{\ln 2} = 0.0014[\mu s]$$

The theoretical value of the time constant is given by

$$\tau_{\text{theo}} = RC.$$

So the uncertainty is

$$u_{\tau_{\text{theo}}} = \sqrt{\left(\frac{\partial}{\partial R} (RC) u_R \right)^2 + \left(\frac{\partial}{\partial C} (RC) u_C \right)^2} = \sqrt{C^2 u_R^2 + R^2 u_C^2}.$$

Here the parameters are given as $R = 99.75\Omega$, $C = 9.984 \times 10^{-8}\text{F}$, $u_C = 10^{-11}\text{F}$, $u_R = 0.01\Omega$, which yield

$$u_{\tau_{\text{theo}}} = 0.10[\mu s]$$

A.2 RL Circuit

The experimental value of the time constant is given by

$$\tau = \frac{T_{1/2}}{\ln 2}.$$

So, the uncertainty is

$$u_\tau = \left| \frac{d}{d(T_{1/2})} \left(\frac{T_{1/2}}{\ln 2} \right) u_{T_{1/2}} \right| = \frac{u_{T_{1/2}}}{\ln 2}.$$

Here the uncertainty of $T_{1/2}$ is $0.01[\mu s]$, so the uncertainty of τ is

$$u_\tau = \frac{0.01}{\ln 2} = 0.014[\mu s]$$

The theoretical value of the time constant is given by

$$\tau_{\text{theo}} = \frac{L}{R}.$$

So the uncertainty is

$$u_{\tau_{\text{theo}}} = \sqrt{\left(\frac{\partial}{\partial R} \left(\frac{L}{R} \right) u_R \right)^2 + \left(\frac{\partial}{\partial L} \left(\frac{L}{R} \right) u_L \right)^2} = \sqrt{\frac{u_L^2}{R^2} + \frac{L^2 u_R^2}{R^4}}.$$

Here the parameters are given as $R = 99.75\Omega$, $L = 0.01\text{H}$, $u_R = 0.01\Omega$, $u_L = 0$, which yield

$$u_{\tau_{\text{theo}}} = 0.010[\mu s].$$

A.3 Uncertainty of Data for RLC Circuit

The experimental value of the time constant is given by

$$\tau = \frac{T_{0.264}}{1.00}.$$

So, the uncertainty is

$$u_\tau = \left| \frac{d}{d(T_{0.264})} \left(\frac{T_{0.264}}{1.00} \right) u_{T_{0.264}} \right| = \frac{u_{T_{1/2}}}{1.00}.$$

Here the uncertainty of $T_{0.264}$ is $0.01[\mu\text{s}]$, so the uncertainty of τ is

$$u_\tau = \frac{0.01}{1.00} = 0.010[\mu\text{s}]$$

The theoretical value of the time constant is given by

$$\tau_{\text{theo}} = \sqrt{LC}.$$

But the uncertainty of L is equal to 0, the uncertainty can be simplified as

$$u_{\tau_{\text{theo}}} = \left| \frac{\partial}{\partial C} (\sqrt{LC}) u_C \right| = \frac{\sqrt{L} u_C}{2\sqrt{C}}.$$

Here $L = 0.01\text{H}$, $C = 99.84\text{nF}$, $u_C = 0.01\text{nF}$, which yield

$$u_{\tau_{\text{theo}}} = 0.0016[\mu\text{s}].$$

A.4 RLC Resonant Circuit

A.4.1 f/f_0

For f/f_0 , the uncertainty is given by

$$u_{f/f_0} = \sqrt{\left(\frac{\partial f/f_0}{\partial f} u_f \right)^2 + \left(\frac{\partial f/f_0}{\partial f_0} u_{f_0} \right)^2} = \sqrt{\left(\frac{u_f}{f_0} \right)^2 + \left(-\frac{f}{f_0^2} u_{f_0} \right)^2}.$$

Take the first set of data as an example,

$$\begin{aligned} u_{f/f_0} &= \sqrt{\left(\frac{u_f}{f_0} \right)^2 + \left(-\frac{f}{f_0^2} u_{f_0} \right)^2} \\ &= \sqrt{\left(\frac{0.001}{5029.000} \right)^2 + \left(-\frac{21420.000}{5029.000^2} \times 0.001 \right)^2} \\ &= 0.0000009. \end{aligned}$$

The rest of the uncertainties are calculated in the same way and are shown in Table 6 following the data of f/f_0 .

A.4.2 I/I_m

For $I/I_m = U_R/U_m$, the uncertainty is given by

$$u_{I/I_m} = \sqrt{\left(\frac{\partial U_R/U_m}{\partial U_R} u_{U_R} \right)^2 + \left(\frac{\partial U_R/U_m}{\partial U_m} u_{U_m} \right)^2} = \sqrt{\left(\frac{u_{U_R}}{U_m} \right)^2 + \left(-\frac{U_R}{U_m^2} u_{U_m} \right)^2}.$$

Take the first set of data as an example,

$$\begin{aligned}
u_{I/I_m} &= \sqrt{\left(\frac{u_{U_R}}{U_m}\right)^2 + \left(-\frac{U_R}{U_m^2} u_{U_m}\right)^2} \\
&= \sqrt{\left(\frac{0.02}{3.90}\right)^2 + \left(-\frac{0.39}{3.90^2} \times 0.02\right)^2} \\
&= 0.005.
\end{aligned}$$

The rest of the uncertainties are calculated in the same way and are shown in Table 6 following the data of I/I_0 .

A.4.3 φ_{theo}

For $\varphi_{\text{theo}} = \tan^{-1} \left(\frac{2\pi f L - \frac{1}{2\pi f C}}{R} \right)$, the uncertainty is given by

$$\begin{aligned}
u_{\varphi_{\text{theo}}} &= \sqrt{\left(\frac{\partial \varphi_{\text{theo}}}{\partial f} u_f\right)^2 + \left(\frac{\partial \varphi_{\text{theo}}}{\partial C} u_C\right)^2 + \left(\frac{\partial \varphi_{\text{theo}}}{\partial R} u_R\right)^2} \\
&= \sqrt{\left(\frac{R(2\pi L + \frac{1}{2\pi f^2 C})}{R^2 + (2\pi f L - \frac{1}{2\pi f C})^2} u_f\right)^2 + \left(\frac{R}{2\pi f C^2 [R^2 + (2\pi f L - \frac{1}{2\pi f C})^2]} u_C\right)^2 + \left(-\frac{2\pi f L - \frac{1}{2\pi f C}}{R^2 + (2\pi f L - \frac{1}{2\pi f C})^2} u_R\right)^2}.
\end{aligned}$$

Take the first set of data as an example, here $f = 21429[\text{kHz}]$, $L = 0.01[\text{H}]$, $C = 99.84[\text{nF}]$, $R = 99.75[\Omega]$, $u_C = 0.01[\text{nF}]$, $u_R = 0.01[\Omega]$, $u_f = 0.001[\text{Hz}]$, which yield

$$u_{\varphi_{\text{theo}}} = 0.0008$$

The rest of the uncertainties are calculated in the same way and are shown in Table 6 following the data of φ_{theo} .

A.4.4 φ_{ex}

For $\varphi_{\text{exp}} = \cos^{-1} \left(\frac{U_R}{U_m} \right)$, the uncertainty is given by

$$u_{\varphi_{\text{ex}}} = \sqrt{\left(\frac{\partial \varphi_{\text{ex}}}{\partial U_R} u_{U_R}\right)^2 + \left(\frac{\partial \varphi_{\text{ex}}}{\partial U_m} u_{U_m}\right)^2} = \sqrt{\left(\frac{-1}{\sqrt{U_m^2 - U_R^2}} u_{U_R}\right)^2 + \left(\frac{U_R}{U_m \sqrt{U_m^2 - U_R^2}} u_{U_m}\right)^2}.$$

Take the first set of data as an example, here $u_U = 0.012[\text{V}]$, $U_m = 3.90[\text{V}]$, $U_R = 0.39[\text{V}]$, which yield

$$u_{\varphi_{\text{exp}}} = 0.005$$

The rest of the uncertainties are calculated in the same way and are shown in Table 6 following the data of φ_{exp} .

Here provides a table of summary of the uncertainties in this part.

	u_{f/f_0}	u_{I/I_m}	$u_{\varphi_{\text{theo}}}$ [rad]	$u_{\varphi_{\text{ex}}}$ [rad]
1	0.005	0.0000009	0.0008	0.005
2	0.005	0.0000005	0.002	0.005
3	0.005	0.0000004	0.003	0.006
4	0.006	0.0000004	0.003	0.006
5	0.006	0.0000003	0.004	0.007
6	0.006	0.0000003	0.005	0.007
7	0.006	0.0000003	0.005	0.009
8	0.007	0.0000003	0.005	0.011
9	0.007	0.0000003	0.004	0.016
10	0.007	0.0000003	0.003	0.020
11	0.007	0.0000003	0.0003	/
12	0.007	0.0000003	0.004	0.020
13	0.007	0.0000003	0.004	0.016
14	0.007	0.0000003	0.005	0.011
15	0.006	0.0000003	0.005	0.009
16	0.006	0.0000003	0.005	0.007
17	0.006	0.0000002	0.004	0.007
18	0.006	0.0000002	0.003	0.006
19	0.005	0.0000002	0.003	0.006
20	0.005	0.0000002	0.002	0.005
21	0.005	0.0000002	0.0014	0.005

Table 9: Uncertainty for φ , f/f_0 and I/I_m .

A.4.5 $f_{0\text{theo}}$

For $f_{0\text{theo}} = \frac{1}{2\pi\sqrt{LC}}$, the uncertainty is given by

$$\begin{aligned} U_{f_{0\text{theo}}} &= \sqrt{\left(\frac{\partial f_{0\text{theo}}}{\partial L} u_L\right)^2 + \left(\frac{\partial f_{0\text{theo}}}{\partial C} u_C\right)^2} \\ &= \sqrt{\left[\frac{1}{2\pi\sqrt{C}} \left(-\frac{1}{2}L^{-\frac{3}{2}}\right) u_L\right]^2 + \left[\frac{1}{2\pi\sqrt{L}} \left(-\frac{1}{2}C^{-\frac{3}{2}}\right) u_C\right]^2} \\ &= \left|\frac{1}{2\pi\sqrt{L}} \left(-\frac{1}{2}C^{-\frac{3}{2}}\right) u_C\right| \end{aligned}$$

Here $L = 0.01$ [H], $C = 99.84$ [nF], $u_C = 0.01$ [nF], which yield

$$u_{\varphi_{\text{theo}}} = 0.3$$

A.4.6 Q_{exp}

For $Q_{\text{exp}} = \frac{f_0}{f_2 - f_1}$, the uncertainty

$$\begin{aligned} u_{Q_{\text{exp}}} &= \sqrt{\left(\frac{\partial Q_{\text{exp}}}{\partial f_0} u_{f_0}\right)^2 + \left(\frac{\partial Q_{\text{exp}}}{\partial f_1} u_{f_1}\right)^2 + \left(\frac{\partial Q_{\text{exp}}}{\partial f_2} u_{f_2}\right)^2} \\ &= \sqrt{\left(\frac{u_{f_0}}{f_2 - f_1}\right)^2 + \left(\frac{f_0}{(f_2 - f_1)^2} u_{f_1}\right)^2 + \left(-\frac{f_0}{(f_2 - f_1)^2} u_{f_2}\right)^2} \end{aligned}$$

Here $f_0 = 5029$ [Hz], $f_1 = 4230$ [Hz], $f_2 = 6000$ [Hz], which yield

$$u_{Q_{\text{exp}}} = 0.000002$$

A.4.7 Q_{theo}

For $Q_{\text{theo}} = \frac{\sqrt{LC}}{RC}$, the uncertainty is given by

$$\begin{aligned} u_{Q_{\text{theo}}} &= \sqrt{\left(\frac{\partial Q_{\text{theo}}}{\partial R} u_R\right)^2 + \left(\frac{\partial Q_{\text{theo}}}{\partial C} u_C\right)^2} \\ &= \sqrt{\left(-\frac{\sqrt{LC}}{R^2 C} u_R\right)^2 + \left(-\frac{\sqrt{L}}{2 R C^{3/2}} u_C\right)^2} \end{aligned}$$

Here $L = 0.01[\text{H}]$, $C = 99.84[\text{nF}]$, $R = 99.75[\Omega]$, $u_C = 0.01[\text{nF}]$, $u_R = 0.01[\Omega]$, which yield

$$u_{Q_{\text{theo}}} = 0.0003$$

B Data Sheet

Please find the original data sheet attached at the end of the report.

UM-SJTU PHYSICS LABORATORY VP241
DATA SHEET (EXERCISE 5)

Name: Haoming Zhu

Student ID: 520021910145

Group: 01

Date: _____

NOTICE. Please remember to show the data sheet to your instructor before leaving the laboratory. The data sheet will not be accepted if the data are recorded with pencil or modified by correction fluid/tape. If a mistake is made in recording a datum item, cancel the wrong value by drawing a fine line through it, record the correct value legibly, and ask your instructor to confirm the correction. Please remember to take a record of the precision of the instruments used. You are required to hand in the original data with your lab report, so please keep the data sheet properly.

$R 99.75 \text{ } \cancel{\text{mV}} \pm 0.01 \text{ } \cancel{\text{mV}}$	$f 1.000 \text{ } \cancel{\text{kHz}} \pm 0.001 \text{ } \cancel{\text{kHz}}$	$E 4.000 \text{ } \cancel{\text{V}} \pm 0.001 \text{ } \cancel{\text{V}}$
$C 99.84 \text{ } \cancel{\text{nF}} \pm 0.01 \text{ } \cancel{\text{nF}}$	$T_{1/2} \cancel{1.44 \text{ ms}} \pm \cancel{0.1 \text{ ms}}$	$7.000 \text{ } \cancel{\text{ms}} \pm 0.001 \text{ } \cancel{\text{ms}}$

Table 1. $T_{1/2}$ measurement data for a RC series circuit.

$R 99.75 \text{ } \cancel{\text{mV}} \pm 0.01 \text{ } \cancel{\text{mV}}$	$f 1.000 \text{ } \cancel{\text{kHz}} \pm 0.001 \text{ } \cancel{\text{kHz}}$	$E 4.000 \text{ } \cancel{\text{V}} \pm 0.001 \text{ } \cancel{\text{V}}$
$L 0.01 \text{ } \cancel{\text{H}} \pm 0 \text{ } \cancel{\text{H}}$	$T_{1/2} \cancel{2.80 \text{ ms}} \pm \cancel{0.01 \text{ ms}}$	$66.00 \text{ } \cancel{\text{ms}} \pm 0.01 \text{ } \cancel{\text{ms}}$

Table 2. $T_{1/2}$ measurement data for a RL series circuit.

$L 0.01 \text{ } \cancel{\text{H}} \pm 0 \text{ } \cancel{\text{H}}$	$C 99.84 \text{ } \cancel{\text{nF}} \pm 0.01 \text{ } \cancel{\text{nF}}$	$E 4.000 \text{ } \cancel{\text{V}} \pm 0.001 \text{ } \cancel{\text{V}}$	$f 1.000 \text{ } \cancel{\text{kHz}} \pm 0.001 \text{ } \cancel{\text{kHz}}$
$T_{0.264} = 59.0 \text{ } \cancel{\text{ms}} \pm 0.01 \text{ } \cancel{\text{ms}}$			

Table 3. $T_{0.264}$ measurement data for a critically damped RLC series circuit.

Instructor's signature: Kee.

$R = 99.75 \Omega \pm 0.01 \Omega$, $L = 0.01 H \pm 0 H$, $C = 99.89 nF \pm 0.01 nF$ $f_0 = 5.029 kHz \pm 0.001 kHz$, $\epsilon = 4.000 V \pm 0.001 V$		
	$U_R [V] \pm 0.01 [V]$	$f [kHz] \pm 0.001 [kHz]$
1	0.39	21.420
2	0.78	11.120
3	1.17	8.600
4	1.56	7.420
5	1.95	6.730
6	2.34	6.300
7	2.73	6.000
8	3.12	5.700
9	3.51	5.450
10	3.66	5.340
11	5.029	3.90
12	3.66	4.710
13	3.51	4.840
14	3.12	4.430
15	2.73	4.230
16	2.34	4.010
17	1.95	3.740
18	1.56	3.400
19	1.17	2.920
20	0.78	2.180
21	0.39	1.090

Table 4. Measurement data for the U_R vs. f dependence for a RLC resonant circuit.

Instructor's signature: _____ 